


AHB Auto Half Barrier Circuit

Based on MKII installation

This document is not endorsed by Network Rail. It is NOT for installation, commissioning, testing or maintenance purposes, it is for information only. Network Rail's own documents must be followed at all times, however; this contains re-written extracts from railway standards.




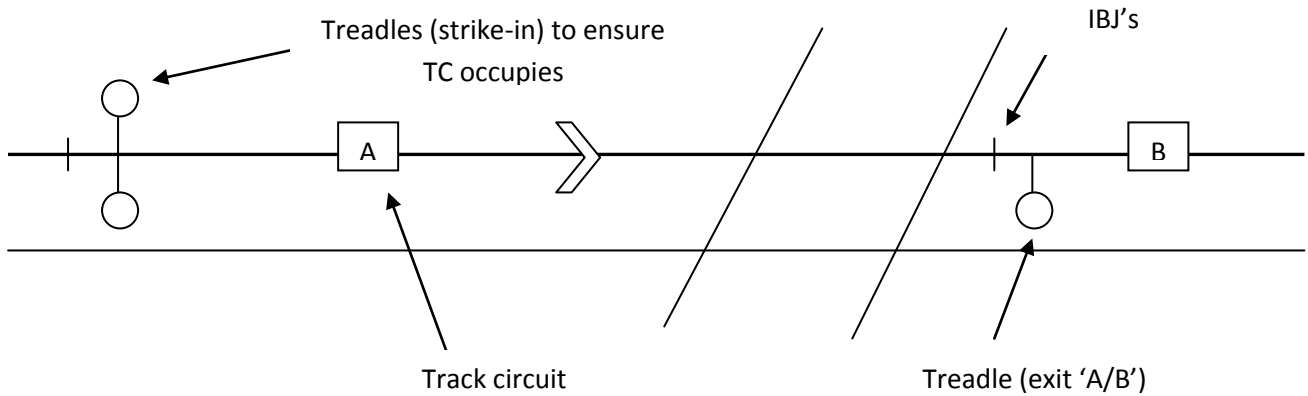AHB – Auto Half Barrier Circuit Page Two of Six




Use the basic track layout above with the following flowchart:


THESE STYLE BOXES DESCRIBE THE FUNCTION OF THE RELAY	THESE STYLE BOXES DESCRIBE THE SEQUENCE OF OPERATION	THESE STYLE BOXES DESCRIBE WHAT IS HAPPENING AT LC & SB
--	--	---

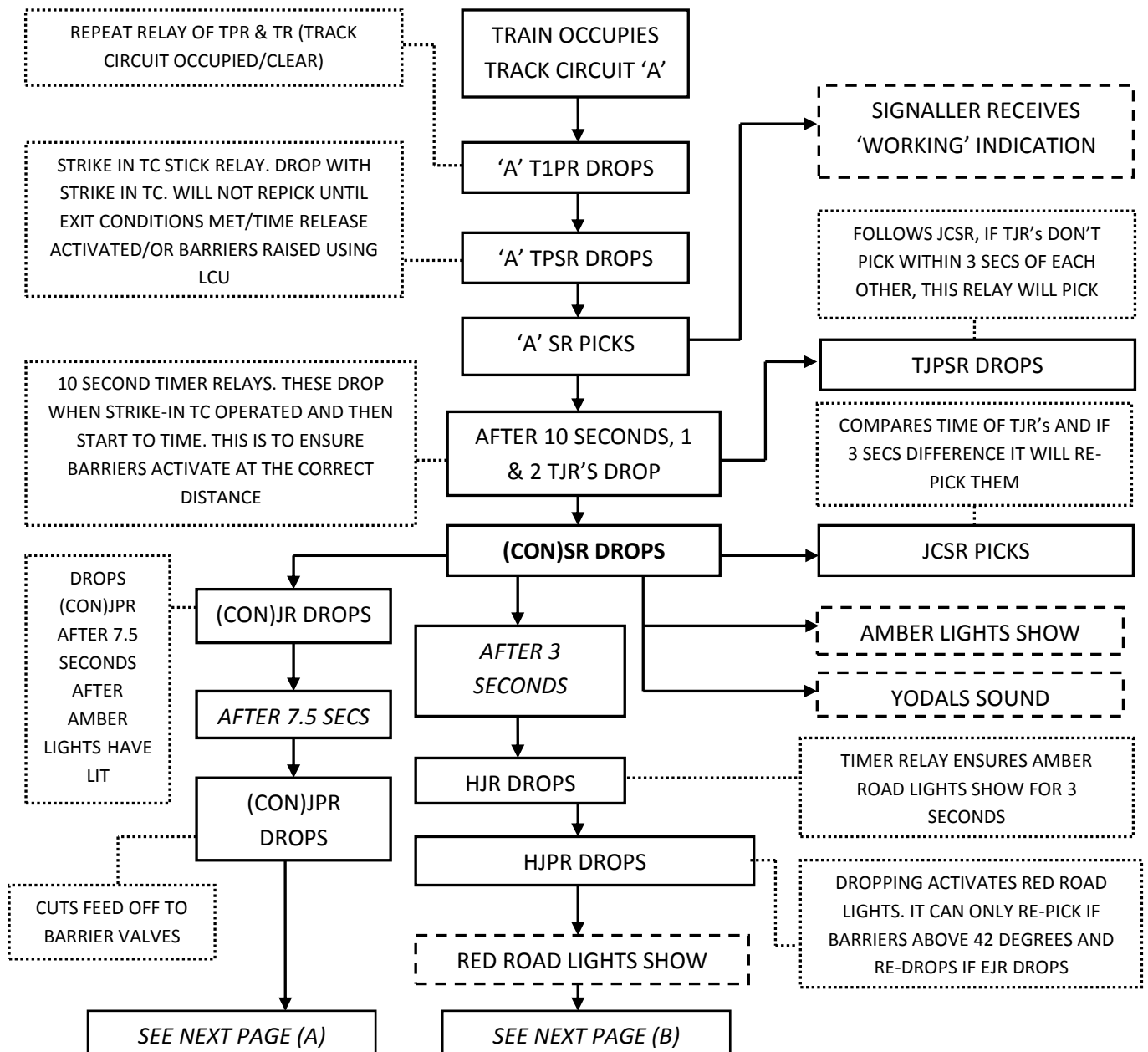

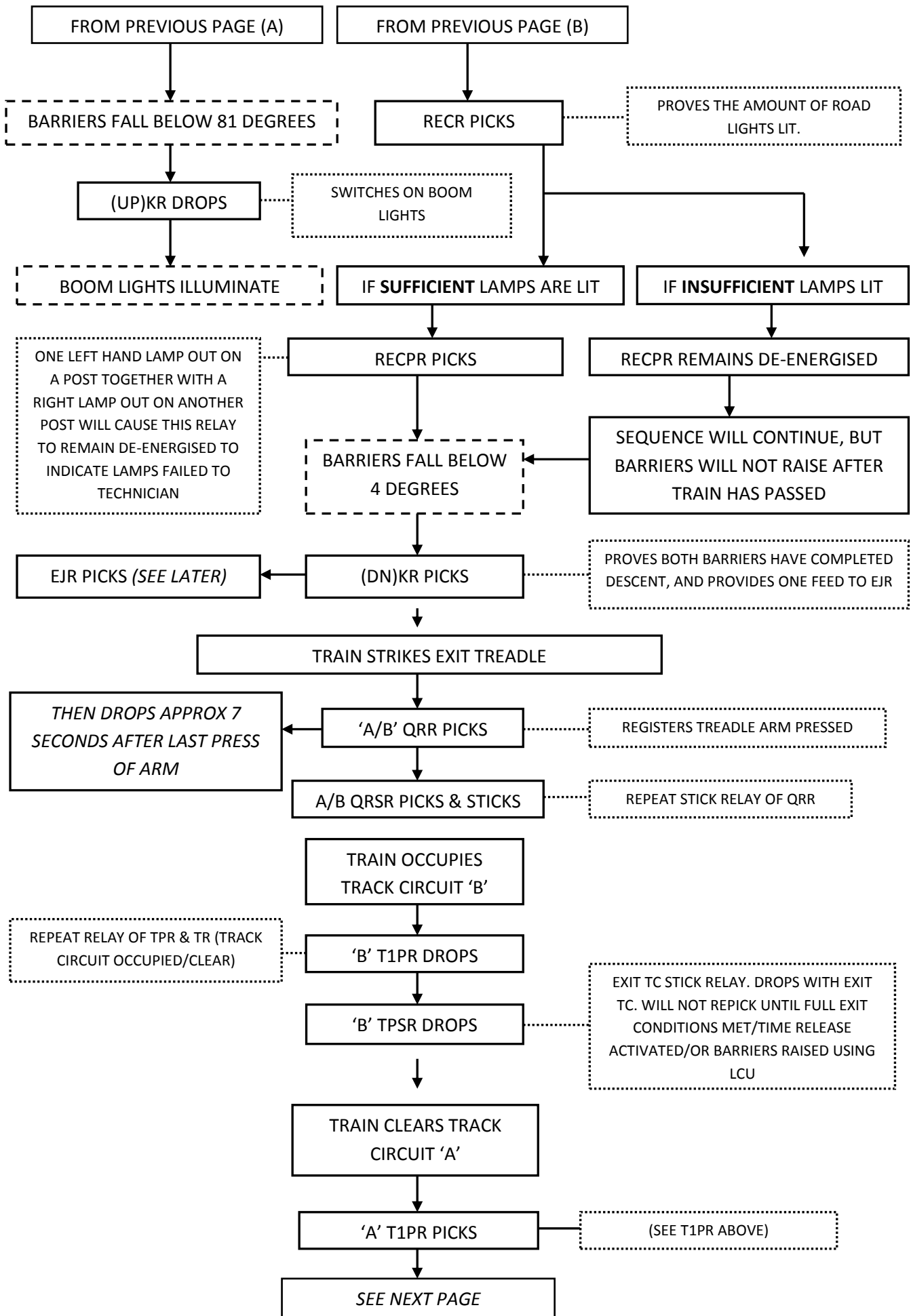
AHB – Auto Half Barrier Circuit Page Three of Six



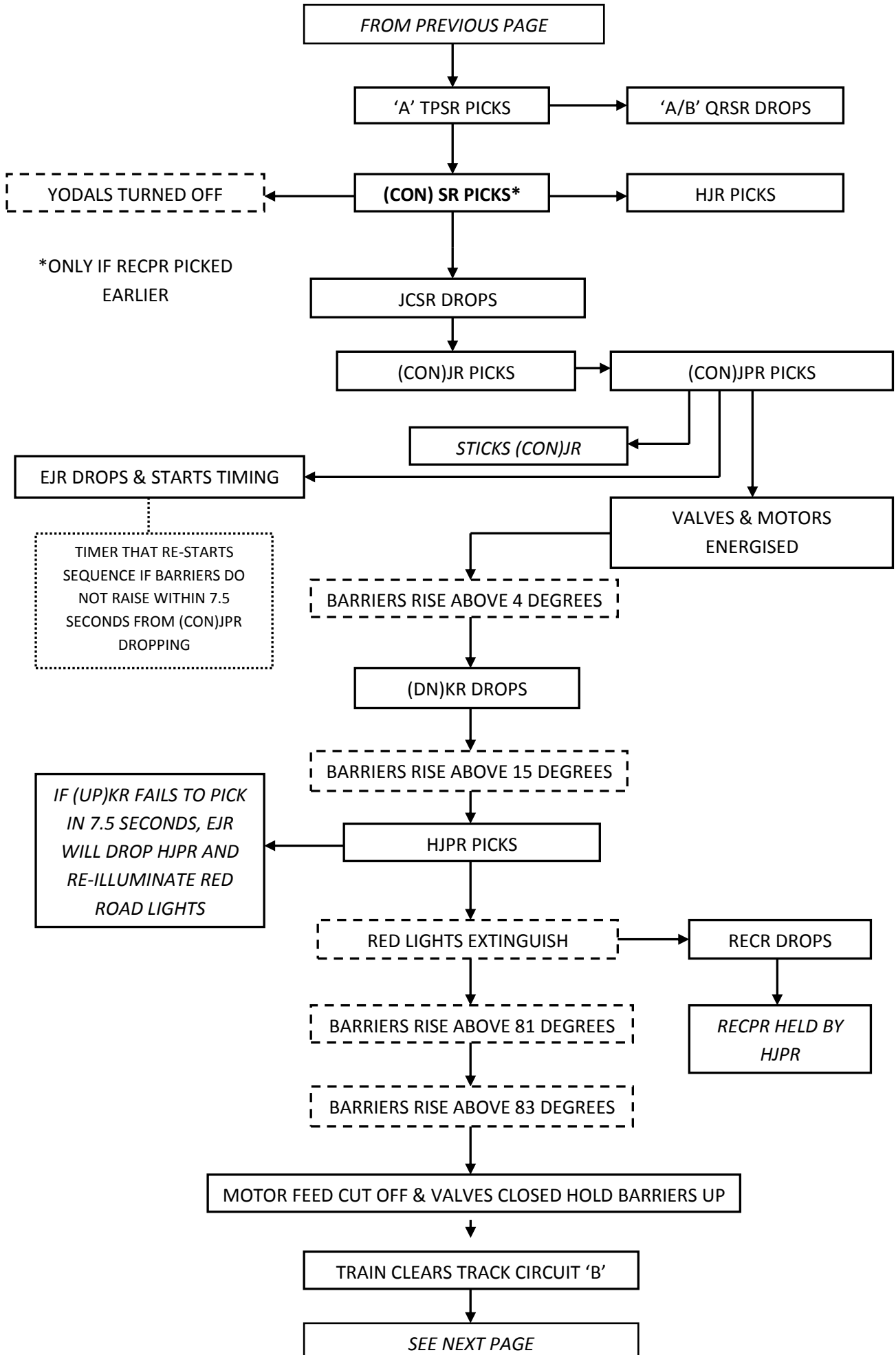AHB – Auto Half Barrier Circuit Page Four of Six



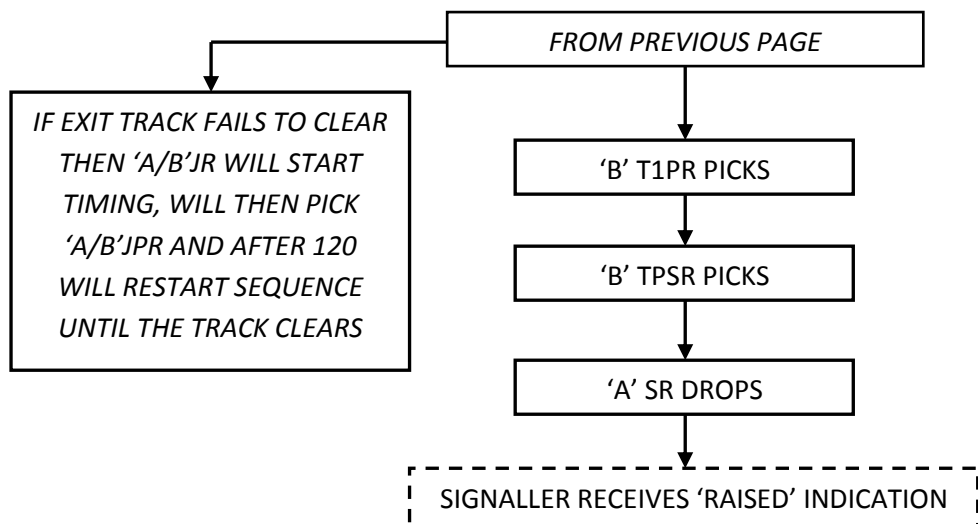AHB – Auto Half Barrier Circuit Page Five of Six



NOTE: IF STRIKE-IN TRACK CIRCUIT FAILS WITHOUT PRESENCE OF A TRAIN, THE SEQUENCE WILL BE INITIATED AND BARRIERS WILL REMAIN DOWN. WHEN THE TRACK CLEARS, THE 'A/B'JR WILL START TO TIME OUT AND PICK 'A/B'JPR, RAISE BARRIERS AND RESTORE BARRIERS RAISED INDICATION. THIS WILL HAPPEN IF TRACKS WERE TESTED ON MAINTENANCE UNLESS THE LC WAS TAKEN ON LOCAL CONTROL, THEN LCU 'UP' CIRCUIT WILL MAINTAIN (CON)SR STICK PATH.

Indication to the signalbox is sent via either three or four wire operation. Three wire uses a common negative, and the other two wires used for 'raised' and 'power off' indication. No voltage gives 'working' indication.

With four wire operation both the negatives are maintained all the time. Only the positive uses one of the two other wires for 'raised power on' and the other wire for 'raised power off', no voltage gives 'working' indication to the signaller.

- **Relay normal positions when crossing normal (barriers raised):**

Relay UP	Relay DOWN
A T1PR	A SR
A TPSR	B SR
B T1PR	A/B QRR
B TPSR	A/B QRSR
(LCU)DOOR CR	A/B JR
(Y/Z)CR (BARRIER DOORS)	A/B JPR
(LCU) (N) CSR (NOT ON LOCAL CONTROL)	(DN)KR
(PO)PR (POWER ON)	JCSR
(UP)KR	EJR
1 TJR	RECR
2 TJR	
(CON)SR	
HJR	
HJPR	

AHB – Auto Half Barrier Circuit Page Six of Six

Relay UP	Relay DOWN
(CON)JR	
(CON)JPR	
RECP	
TJPSR	

- **Relays not mentioned in flowchart above:**

(CON)YR	Combines the directional controls for all four approaches on double-line bi-directional AHB's.
ZCSR	Prevents sequence of road lights if LCU lower/hand switch is turned with barriers up and either pedestal door open or Y/Z(DOOR)CR has failed.
TZSR	Track special relay used for a berth track for a regulated signal. Once dropped it requires overrun track circuit occupied or a treadle activated. It is used to prevent a train disappearing due to rusty rails.
TZJR	Timer used for above relay.
(UP) QRCSR or (DN)QRCSR	Used in conjunction with QRSR, it proves the treadle for direction it states has been normalised after passage of a train
(NS)R	Non-stopping train repeat of button in SB
(NS)SR	Stick relay for above
(DWL)R	Drivers white relay
(DWL)ECR	Drivers white light proving relay

- **Differences between Mark I and Mark II installations:**

Mark One	Mark Two
'Penguin' style pedestal mounted on a concrete pillar, with metal framework, hydraulic power pack with hoses. Removable top and bottom very flimsy plastic covers (called guillotine covers).	One piece steel '843 type' pedestal with two hinged access doors and microswitch on handle side. Contains sealed hydraulic power pack. But better weather protection compared with a Mark One.
LCU inside one of the pedestals, with push buttons and lever over auto button.	LCU in post near one of the pedestals containing three-position switch.
Road lights and bells (later Yodals) fixed to same concrete post as the pedestals.	All four road lights have their own post. Two yodals fixed to two posts.
Barrier booms made from wood.	Barrier booms made from tubular metal.
Barrier weights inside pedestals.	Barrier weights on end of barriers.
Earlier installations had neon 'Another Train Coming' signs (later abolished).	Another Train Coming signs are metal retro reflective type.
Telephones to signalbox inside flap on pedestals.	Telephones on their own posts.
Relay (CON)R used.	Relay changed to a stick relay [(CON)SR]
ECR's used in light circuits.	RECR relays used.
The circuitry between both varies with some relays abolished/added.	

>>>END<<<